S1	S0	
0	0	load
0	1	shift left
1	0	shift right
1	1	save

← I have the muxes like this b/c I drew the connections incorrectly at first. It should still operate correctly in this fashion

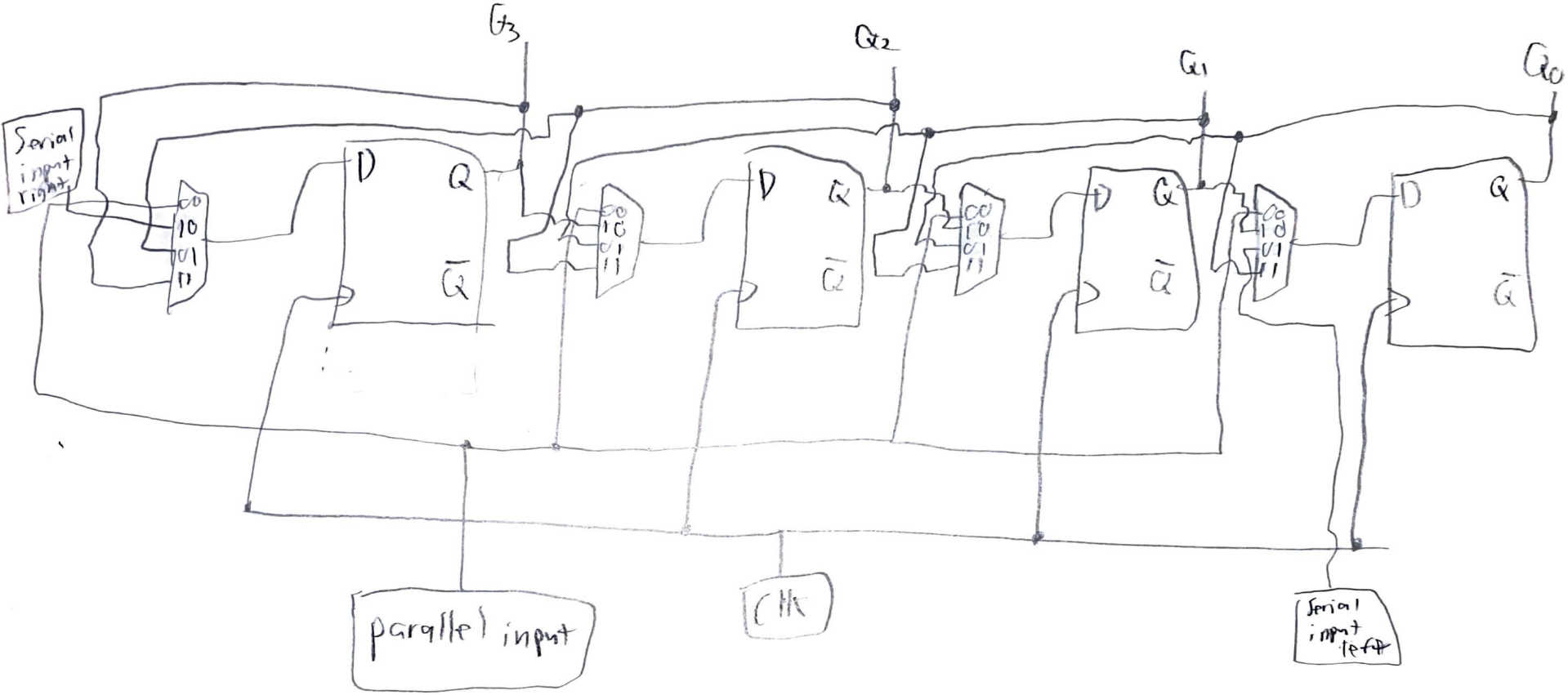

Dylan Thornby